

Electrical Principles

Randy Brack, N5MRB – n5mrb@arrl.net

1. Introduction
2. Coordinate systems
 - A. Rectangular coordinates
 - i. Origin, X and Y
 - a. **The two numbers that are used to define a point on a graph using rectangular coordinates represent the coordinate values along the horizontal and vertical axes.** [E5C11]
 - ii. Complex coordinates
 - a. Imaginary numbers i and j
 - b. $1/j = -j$
 - c. $X + jY$
 - iii. Resistive and reactive
 - a. Horizontal and vertical axes
 - b. **In rectangular coordinates, the horizontal axis represents the resistive component.** [E5C09]
 - c. **In rectangular coordinates, the vertical axis represents the reactive component.** [E5C10]
 - d. **The rectangular coordinate system is often used to display the resistive, inductive, and/or capacitive reactive components of impedance.** [E5C13]
 - e. Inductive (top) and capacitive (bottom) $Z = R + jX$
 - f. **Capacitive reactance in rectangular notation is represented by $-jX$.** [E5C01]
 - g. Oh, I see (OIC) rule
 - h. **If you plot the impedance of a circuit using the rectangular coordinate system and find the impedance point falls on the right side of the graph on the horizontal axis, the circuit is equivalent to a pure resistance.** [E5C12]
 - i. **Impedance $50 - j25$ represents 50 ohms resistance in series with 25 ohms capacitive reactance.** [E5C06]
 - B. Calculating impedance
 - i. **$X_L = 2\pi fL$** to calculate inductor's reactance
 - a. **Series circuit consisting of a 300 ohm resistor and an 18 microhenry inductor at 3.505 MHz ($300 + j400$) (Example 4.4) [E5C15]**
 - ii. **$X_C = \frac{1}{2\pi fC}$** to calculate capacitor's reactance
 - a. **Series circuit consisting of a 400 ohm resistor and a 38 picofarad capacitor at 14 MHz ($400 - j300$) (Example 4.6) [E5C14]**
 - b. **Series circuit consisting of a 300 ohm resistor and a 19 picofarad capacitor at 21.200 MHz ($300 - j400$) (Example 4.7) [E5C16]**
 - c. **Series circuit consisting of a 300 ohm resistor, a 0.64 microhenry inductor and an 85 picofarad capacitor at 24.900 MHz ($300 + j100 - j75 = 300 + j25$) (Example 4.8) [E5C17]**
 - C. Polar coordinates
 - i. Scalars and vectors
 - ii. A vector has magnitude and direction
 - iii. They're called polar coordinates because it's like looking at the earth from the north pole

Electrical Principles

- iv. $r \angle \theta$ [or (r, θ)]
- v. **In polar coordinates, a vector has both magnitude and an angular component.** [E5C07]
- vi. Inductive/capacitive reactance on graph
- vii. **Impedances are described by phase angle and amplitude.** [E5C02]
- viii. **The polar coordinate system is often used to display the phase angle of a circuit containing resistance, inductive and/or capacitive resistance.** [E5C08]
- ix. **In polar coordinates, a positive phase angle represents an inductive reactance.** [E5C03]
- x. **In polar coordinates, a negative phase angle represents a capacitive reactance.** [E5C04]
- xi. **A phasor diagram shows the phase relationship between impedances at a given frequency.** [E5C05]

D. Basic trigonometry

- i. Triangles
- ii. $\sin, \cos, \tan, \sin^{-1}, \cos^{-1}, \tan^{-1}$ ($\cos 30^\circ = 0.866$; $\cos 45^\circ = 0.707$; $\cos 60^\circ = 0.5$; $\tan 45^\circ = 1.0$)
- iii. Chief SOHCAHTOA

E. Converting between rectangular and polar coordinates

i. Polar to rectangular

- a. $r \angle \theta \rightarrow (a + jb)$ **Example: $10 \angle 30^\circ \rightarrow ?$**
- b. $a = r \cos \theta = 10 * 0.866 = 8.7$ (rounded)
- c. $b = r \sin \theta = 10 * 0.5 = 5$ **? = $8.7 + j5$**

ii. Rectangular to polar

- a. $(a + jb) \rightarrow r \angle \theta$ **Example: $3 + j3 \rightarrow ?$**
- b. $r = \sqrt{(a^2 + b^2)} = \sqrt{(3^2 + 3^2)} = \sqrt{18} = 4.2$ (rounded)
- c. $\theta = \tan^{-1}\left(\frac{b}{a}\right) = \tan^{-1}\left(\frac{3}{3}\right) = \tan^{-1}(1) = 45^\circ$
? = $4.2 \angle 45^\circ$

3. Electromagnetic fields

- A. **E/M field (or electrostatic field) stores potential energy.** [E5D08]
- B. **Strength of magnetic field around a conductor is determined by amount of current flowing through the conductor.** [E5D07]
- C. **Orientation around the conductor is determined by left hand rule using electron flow (electronic current).** [E5D06]

4. Time constants and phase relationships

- A. RLC Time constants [see graph, p. 4-10]
 - i. **Time required for the capacitor in an RC circuit to be charged to 63.2% of the applied voltage is one time constant.** [E5B01]
 - ii. **Time it takes for a charged capacitor in an RC circuit to discharge to 36.8% of its initial voltage is one time constant.** [E5B02]
 - iii. $\tau = RC$ [resistance in ohms, capacitance in farads]
 - iv. See p. 4-13 for formulas for R_T and C_T , both series and parallel.
 - v. **What is the time constant for a circuit having two 220 microfarad capacitors and two 1 megohm resistors, all in parallel? 220 seconds** [E5B04] Example on p. 4-13
 - vi. Curve for current buildup in RL circuit is identical to voltage curve for charging capacitor

Electrical Principles

- B. Phase angles between voltage and current
 - i. See Figure 4.14 on p. 4-15. Remember ICE.
 - ii. **Current through a capacitor leads the applied voltage by 90°.** [E5B09]
 - iii. See Figure 4.17 on p. 4-16. Remember ELI the ICE man.
 - iv. **Voltage applied to an inductor leads the current through it by 90°.** [E5B10]
 - v. **What is the phase angle between the voltage across and the current through a series RLC circuit if XC is 500 ohms, R is 1 kilohm, and XL is 250 ohms? 14 degrees with the voltage lagging the current.** [E5B07]
 - vi. **What is the phase angle between the voltage across and the current through a series RLC circuit if XC is 100 ohms, R is 100 ohms, and XL is 75 ohms? 14 degrees with the voltage lagging the current.** [E5B08]
 - vii. **What is the phase angle between the voltage across and the current through a series RLC circuit if XC is 25 ohms, R is 100 ohms, and XL is 50 ohms? 14 degrees with the voltage leading the current.** [E5B11]
- 5. Admittance and susceptance
 - A. Measured in Siemens (S)
 - B. Reciprocals (inverse)
 - i. Resistance → conductance (G)
 - ii. **Impedance → admittance (Y)** [E5B12]
 - iii. **Reactance → susceptance (B)** [E5B06]
 - iv. **The letter B is commonly used to represent susceptance.** [E5B13]
 - v. These are also reciprocals in magnitude
 - vi. **What happens to the magnitude of a reactance when it is converted to a susceptance? The magnitude of the susceptance is the reciprocal of the magnitude of the reactance.** [E5B05]
 - vii. Change sign of a phase angle when taking its reciprocal
 - viii. **What happens to a phase angle of a reactance when it is converted to a susceptance? The sign is reversed.** [E5B03]
 - ix. Reciprocals can also be written in either rectangular or polar form
- 6. Reactive power and power factor
 - A. Reactive power
 - i. Resistive part of the circuit consumes and dissipates power as heat
 - ii. **In an AC circuit with ideal inductors and capacitors, reactive power is repeatedly exchanged between the associated magnetic and electric fields, but is not dissipated.** [E5D09]
 - iii. **Reactive power is therefore wattless, nonproductive power.** [E5D14]
 - B. Power factor
 - i. $PF = \frac{P_{REAL}}{P_{APPARENT}}$ and ranges from 0 to 1. Power is consumed by resistance.
 - a. If PF =1, voltage & current are in phase and all apparent power is real power
 - b. If PF = 0, voltage & current are 90° out of phase and all apparent power is reactive power
 - ii. $P_{REAL} = P_{APPARENT} \times PF$
 - a. **How can the true power be determined in an AC circuit where the voltage and current are out of phase? By multiplying the apparent power times the power factor.** [E5D10]
 - b. (Example 4.16 on p. 4-28:) **How many watts are consumed in a circuit having a power factor of 0.71 if the apparent power is 500 VA? 355 W** [E5D18]

Electrical Principles

- iii. Phase angle: $PF = \cos \theta$
 - a. **What is the power factor of an R-L circuit having a θ phase angle? [$\cos 30^\circ = 0.866$; $\cos 45^\circ = 0.707$; $\cos 60^\circ = 0.5$] [E5D11, E5D15, E5D16]**
 - iv. $P = I E$ (current times voltage)
 - a. (Example 4.13 on p. 4-27:) **How many watts are consumed in a circuit having a power factor of 0.2 if the input is 100 VAC at 4 amperes? 80 watts [E5D12]**
 - b. (Example 4.15 on p. 4-28:) **How many watts are consumed in a circuit having a power factor of 0.6 if the input is 200 VAC at 5 amperes? 600 watts [E5D17]**
 - v. $P = I^2 R$ for a series circuit, where I is RMS current [Twinkle, twinkle, little star]
 - a. (Example 4.14 on p. 4-27:) **How much power is consumed in a circuit consisting of a 100 ohm resistor in series with a 100 ohm inductive reactance drawing 1 ampere? 100 watts [E5D13]**
 - vi. $P = E^2/R$ for a parallel circuit, where E is the RMS voltage
7. Skin effect and conductor length
- A. Skin effect due to frequency increase
 - i. With frequency increase, EM fields of signals don't penetrate as deeply into a conductor such as a wire
 - ii. At dc, the whole cross-section of the wire carries current, but with **increasing frequency, the current is confined to regions closer and closer to the surface of the wire, shrinking the effective area.** [E5D01]
 - B. Conductor length
 - i. Want to avoid unexpected and unwanted **parasitic inductance** in leads, **increases with frequency.** [E5D05]
 - ii. Even #24 AWG wire has an inductance of about 20 nH per inch of length
 - iii. **To avoid unwanted inductive reactance in circuits used for VHF and above, keep lead lengths short.** [E5D02]
 - iv. **At microwave frequencies, short leads reduce phase shifts along the connection.** [E5D04]
 - v. **Microstrip are precision printed circuit conductors above a ground plane that provide constant impedance interconnects at microwave frequencies.** [E5D03]
8. Resonant circuits
- A. Resonant frequency
 - i. **Resonance in an electrical circuit is the frequency at which the capacitive reactance equals the inductive reactance.** [E5A02]
 - ii. Circuit is resonant when the inductive reactance value is the same as the capacitive reactance value, regardless of series or parallel
 - iii. **Resonance can cause the voltage across reactances in series to be larger than the voltage applied to them.** [E5A01]
 - iv. Because the voltages across the inductor and capacitor cancel each other out, **the magnitude of the impedance of a series (or parallel) RLC circuit at resonance is approximately equal to the circuit resistance.** [E5A03, E5A04]
 - v. Resonant frequency: $f_r = \frac{1}{2\pi\sqrt{LC}}$
 - vi. Example following equation 4.13 on p. 4-29. Note exponents and resistance. **What is the resonant frequency of a series RLC circuit if R is 22 ohms, L is 50 microhenries, and C is 40 picofarads? 3.56 MHz.** [E5A14]

Electrical Principles

- vii. Example at top of p. 4-30. **What is the resonant frequency of a parallel RLC circuit if R is 33 ohms, L is 50 microhenries, and C is 10 picofarads? 7.12 MHz.** [E5A16]
- B. Impedance vs. Frequency
- As mentioned earlier, at resonance, impedance approximates the circuit resistance for both series and parallel circuits
 - For both series and parallel RLC circuits at resonance**, because inductive and capacitive reactance are equal but opposite, they cancel each other out, and resulting **current and voltage are in phase.** [E5A08]
 - Current reaches maximum at resonant frequency at the input of a series-resonant circuit.** [E5A05]
 - For a parallel RLC circuit at resonance, the input current is minimum,** [E5A07] **but the circulating current is maximum** [E5A06] because of energy exchange between inductor and capacitor
9. Q (Quality factor)
- A. $Q = X/R$
- One definition of Q is the ratio of reactance to resistance in a circuit
 - The lower the resistive losses, the higher the Q.** [E5A15]
- B. $Q_{\text{SERIES}} = \frac{1}{R} \sqrt{\frac{L}{C}}$ or $Q_{\text{SERIES}} = X/R$
- How is the Q of an RLC series resonant circuit calculated? Reactance of either the inductance or capacitance divided by the resistance.** [E5A10]
- C. $Q_{\text{PARALLEL}} = R \sqrt{\frac{C}{L}}$ or $Q_{\text{PARALLEL}} = R/X$
- How is the Q of an RLC parallel resonant circuit calculated? Resistance divided by the reactance of either the inductance or capacitance.** [E5A09]
- D. **As Q increases in a resonating circuit, so do internal voltages and circulating currents.** [E5A13]
10. Half-power bandwidth
- Describe half-power points f_1 and f_2 in Figure 4.29 on p. 4-33
 - Half-power bandwidth Δf = difference between f_1 and f_2
 - The higher the Q, the sharper the resonant circuit's frequency response
 - Half-power bandwidth $\Delta f = \frac{f_r}{Q}$
 - Examples at bottom of p. 4-33 and top of 4-34
- What is the half-power bandwidth of a parallel resonant circuit that has a resonant frequency of 7.1 MHz and a Q of 150? 47.3 kHz.** [E5A11]
 - What is the half-power bandwidth of a parallel resonant circuit that has a resonant frequency of 3.7 MHz and a Q of 118? 31.4 kHz.** [E5A12]
11. Impedance matching circuits (p. 4-34)
- Transform one ratio of voltage to current (impedance) at the output to another at the input
 - Again, as Q increases, internal voltages and currents increase
 - As Q increases, matching bandwidth decreases,** [E5A17] like that of a resonant circuit